

4.18

(1) 一位全加器

设输入为 A 、 B 、 C_{in} 输出为 F_o C_{out}

功能表为


A	B	C_{in}	F_o	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$F_o = \overline{A}\overline{B}C_{in} + \overline{A}B\overline{C}_{in} + A\overline{B}\overline{C}_{in} + ABC_{in}$$

$$= \overline{\overline{A}B\overline{C}_{in} \overline{A}B\overline{C}_{in} \overline{A}B\overline{C}_{in} \overline{A}B\overline{C}_{in}}$$

$$C_{out} = \overline{A}BC_{in} + A\overline{B}C_{in} + AB\overline{C}_{in} + ABC_{in}$$
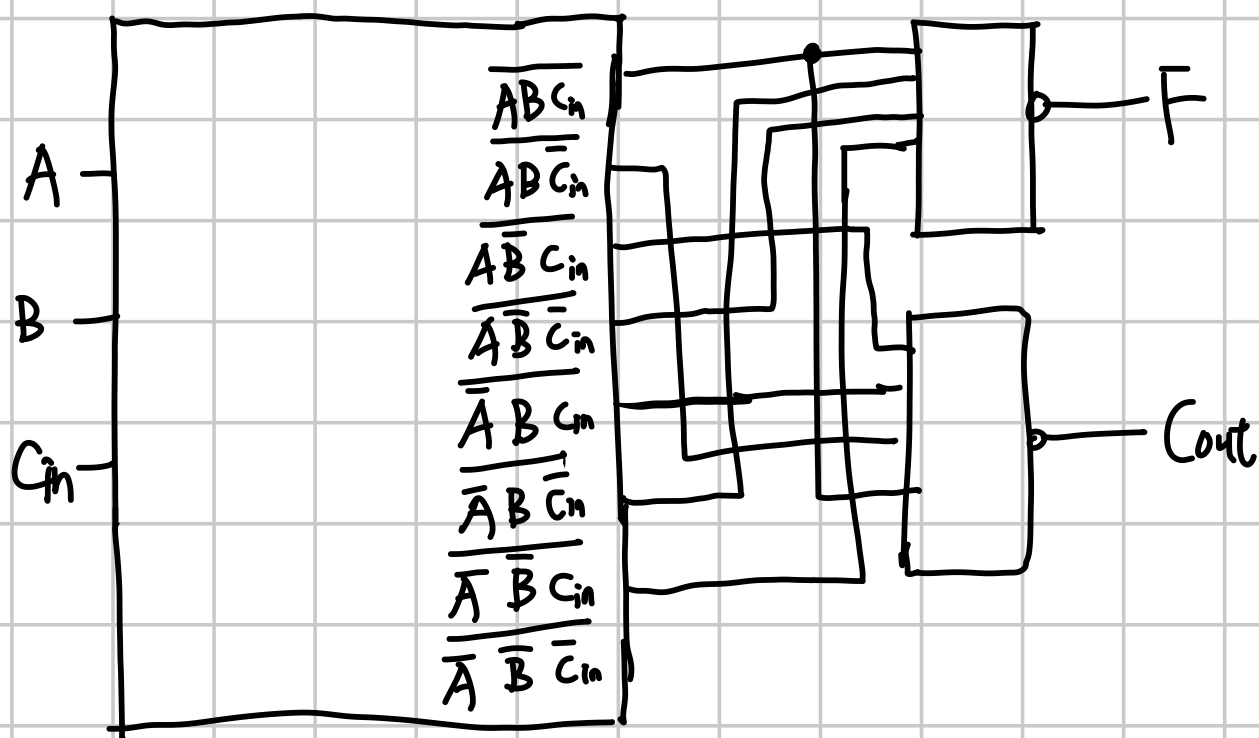
$$= \overline{\overline{A}BC_{in} \overline{A}BC_{in} \overline{A}BC_{in} \overline{A}BC_{in}}$$



一位全减器, $A-B$.

功能表为


A	B	C_{in}	F	C_{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$F = \overline{A}\overline{B}C_{in} + \overline{A}B\overline{C}_{in} + A\overline{B}\overline{C}_{in} + ABC_{in}$$

$$= \overline{\overline{A}\overline{B}C_{in} \overline{A}B\overline{C}_{in} A\overline{B}\overline{C}_{in} ABC_{in}}$$

$$C_{out} = \overline{A}BC_{in} + \overline{A}B\overline{C}_{in} + \overline{A}BC_{in} + ABC_{in}$$
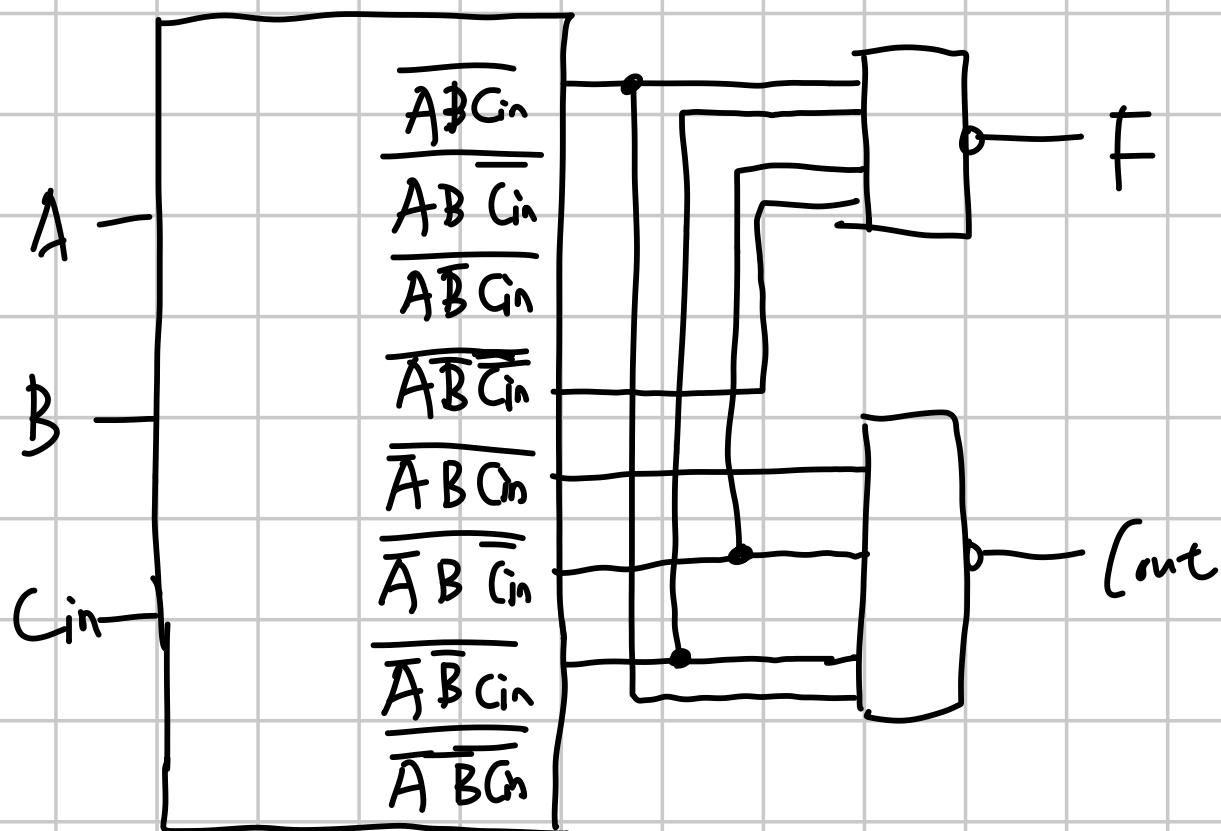
$$= \overline{\overline{A}BC_{in} \overline{A}B\overline{C}_{in} \overline{A}BC_{in} ABC_{in}}$$




4.23

由 4.18 可知,

$$S = ABC_{i-1} + A\bar{B}\bar{C}_{i-1} + \bar{A}B\bar{C}_{i-1} + \bar{A}\bar{B}C_{i-1}$$
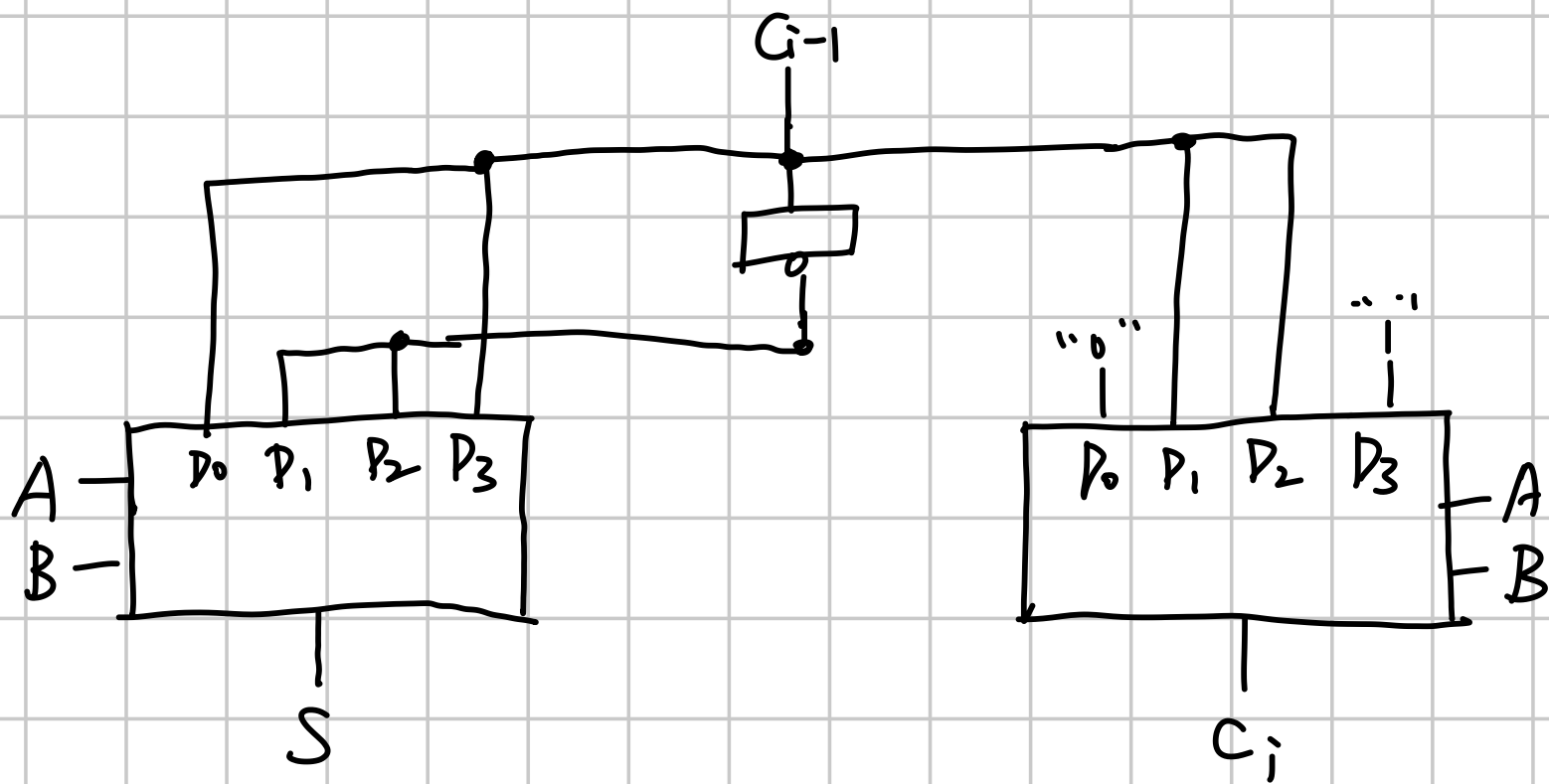
$$C_i = \bar{A}BC_{i-1} + A\bar{B}C_{i-1} + AB\bar{C}_{i-1} + ABC_{i-1}$$



附加题

① 1位全加器构成16位串行加法器。

用(c)型和(d)型一级全加器交叉串联形成16位全加器应该是同类型中最快的

即(c)的 $\bar{C}_n$ 输出到(d)中, (d)的 C_n 输出到(c)中。

已知(c)(d)型一位全加器单独获得 C 、 F 的门延时分别为2级、3级

(c)型全加器获得 $\bar{C}$ 需一级门延时, 可知

$$C_1 = 2 \quad F_1 = 3$$

$$F_i = C_i + 1$$

$$C_i = \bar{C}_{i-1} + 1 = C_{i-1}$$

$$C_{i+1} = C_i + 2$$

$$\text{得 } C_i = \left\lfloor \frac{i+1}{2} \right\rfloor \times 2$$

$$C_{16} = 16$$

$$F_{16} = C_{16} + 1 = 17$$

∴ 1位全加器串联形成的最快的16位串行加法器的门延时为 $C_{16} = 16$
 $F_{16} = 17$

② 4位并行全加器构成16位串行全加器

4位并行全加器 C_i 延迟级数与位数无关, 都是2级。

F_i 基本都是3级

用4片四位并行全加器组成16位加法器,

片间进位串行逐片传递

$$\therefore C_1 \sim C_4 = 2 \quad F_1 \sim F_4 = 3$$

$$C_5 = (C_4 + 2) = 4 \quad F_5 = C_5 + 1 = 5$$

$$C_5 \sim C_8 = 4 \quad F_5 \sim F_8 = 5$$

$$C_9 = (C_8 + 2) = 6$$

$$F_9 = C_9 + 1 = 7$$

$$C_9 \sim C_{12} = 6$$

$$F_9 \sim F_{12} = 7$$

$$C_{13} = C_{12} + 2 = 8$$


$$F_{13} = C_{13} + 1 = 9$$

$$C_{13} \sim C_{16} = 8$$

$$F_{13} \sim F_{16} = 9$$

最终结果 $F_{11} = 9 \quad C_{16} = 8$

③ 16位并行加法器

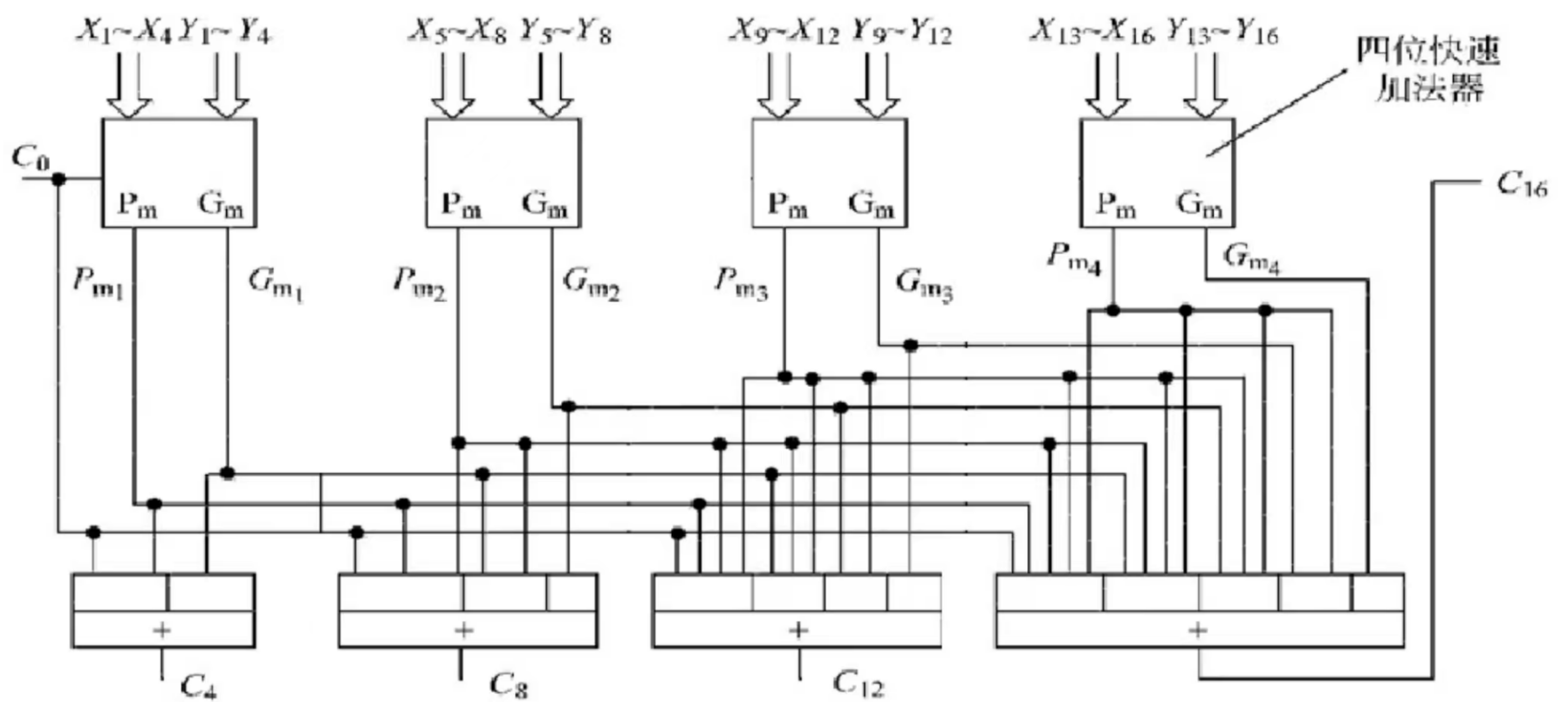

四位并行加法器的输出提供 P_m , G_m . 需2级延迟. F 需3级延迟

$$\therefore C_4 = C_8 = C_{12} = C_{16} = 2 + 1 + 3 = 6 \text{ 级延迟}$$

$$F_1 \sim F_4 = 3 \quad F_5 \sim F_8 = C_4 + 3 = 6$$

$$F_9 \sim F_{12} = C_8 + 3 = 6 \quad F_{13} \sim F_{16} = C_{12} + 3 = 6$$

$$\therefore C_{16} = 6 \quad F_{16} = 6$$